

# Digital systems and basics of electronics

Adam Szmigielski


aszmigie@pjwstk.edu.pl

materials: *ftp(public) : //aszmigie/SYC/ENG*


# Designing of Sequential Circuits - lecture 10

## Combinational and sequential circuits

układ kombinacyjny

 

układ sekwencyjny

 


## Internal state

*In a sequential circuit there are internal states.*

- *Internal states* or (shorter *states*) "keep within limits" possibility of system change (evolution), because the future value of state depends on current state and value of inputs,
- System behavior is modelled by *directed graph* - with each *node* is associated *state* and *value of outputs*, each *arrow* determinates *next state* under the influence of current *input*,
- With each *internal state* are associated value of outputs,
- It is possible that *state* can not be measured externally (IN/OUT model of system),
- In *sequential circuits* state is modelled by *flip-flops* and combinational elements.

## State diagram - transfer graph

 

Directed graph models behavior of sequential circuit (*mod7* counter).


## State coding

$S_t$	$S_{t+1}$	$Y_t$
$S_0$	$S_1$	0
$S_1$	$S_2$	1
$S_2$	$S_3$	2
$S_3$	$S_4$	3
$S_4$	$S_5$	4
$S_5$	$S_6$	5
$S_6$	$S_0$	6


coding	$S_t$	$S_{t+1}$	$Y_t$
$S_0 \rightarrow 000$	000	001	000
$S_1 \rightarrow 001$	001	010	001
$S_2 \rightarrow 010$	010	011	010
$S_3 \rightarrow 011$	011	100	011
$S_4 \rightarrow 100$	100	101	100
$S_5 \rightarrow 101$	101	110	101
$S_6 \rightarrow 110$	110	000	110

## Mealy's and Moore's state machines

automat Mealy'ego

 

automat Moore'a

 

Circuit ( $\lambda$ ) realizing *output function* is a combinational circuit and block ( $\delta$ ) realizes memory (*excitation function*).

$$\begin{cases} x(k+1) = \delta(x(k), u(k)) & \text{state equation: } \delta - \text{excitation function} \\ y(k) = \lambda(x(k), u(k)) & \text{output equation: } \lambda - \text{output function} \end{cases}$$

## Clock



- The sequence of states is important in sequential circuits,
- Additional signal called *clock* is used to synchronize changes,
- Clock activated with *positive slope* are mainly used.



# Designing of Sequential Circuits

## Design stages

We focus on *Moore's state machine* design.

*Main steps* of system synthesis:

1. **Step 1:** Diagram design - directed graph models system behavior. *Node* represents *state* and *value of outputs*, each *arrow* determinates *next state* under the influence of current *input*. *Deterministic state machine* for each state must take into account all combination of inputs.
2. **Step 2:** State coding - use the smallest number of variables (1 bit 1 flip-flop).
3. **Step 3:** Excitation function - for each flip-flop we need to find signal given on flip-flop inputs.
4. **Step 4:** Output function - for each output draw the Karnaugh map and find output function - mapping *internal stages* into outputs.

## Example

Task:

Design two inputs  $x_1, x_2$  and two outputs  $y_1, y_2$  sequential circuit working as follow:

1. If both inputs are ones ( $x_1 = 1, x_2 = 1$ ) then both outputs  $y_1, y_2$  periodically shout be switched on and off (sequence  $00 \rightarrow 11 \rightarrow 00$ ),
2. Two zeros on inputs ( $x_1 = 0, x_2 = 0$ ) should switch off outputs ( $y_1 = 0, y_2 = 0$ ),
3. The rest input combinations cause that outputs follow *mod3* counter.

## Determination of states - state diagram


Because outputs  $y_1, y_2$  can reach all combinations (00, 01, 10 and 11) we need at least 4 states.

For state  $S_0$ :  $y_1 = 0$  i  $y_2 = 0$

For state  $S_1$ :  $y_1 = 0$  i  $y_2 = 1$

For state  $S_2$ :  $y_1 = 1$  i  $y_2 = 0$

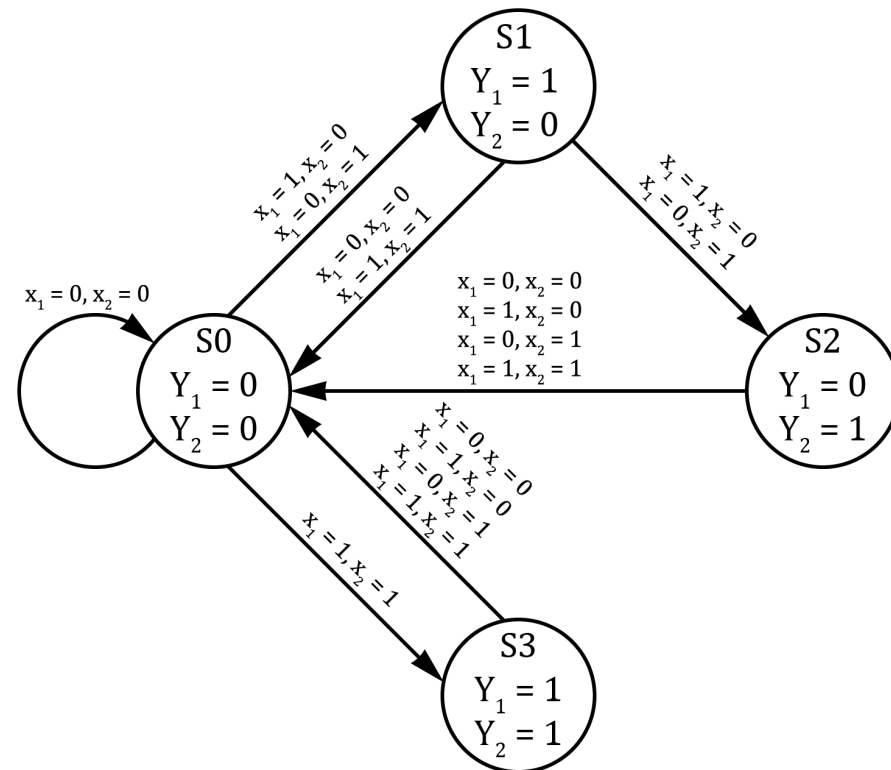
For state  $S_3$ :  $y_1 = 1$  i  $y_2 = 1$



## State table and state diagram

$S^{t+1}$  :

$S^t \backslash x_2, x_1$	00	01	11	10	$y_2, y_1$
$S_0$	$S_0$	$S_1$	$S_3$	$S_1$	00
$S_1$	$S_0$	$S_2$	$S_0$	$S_2$	01
$S_2$	$S_0$	$S_0$	$S_0$	$S_0$	10
$S_3$	$S_0$	$S_0$	$S_0$	$S_0$	11

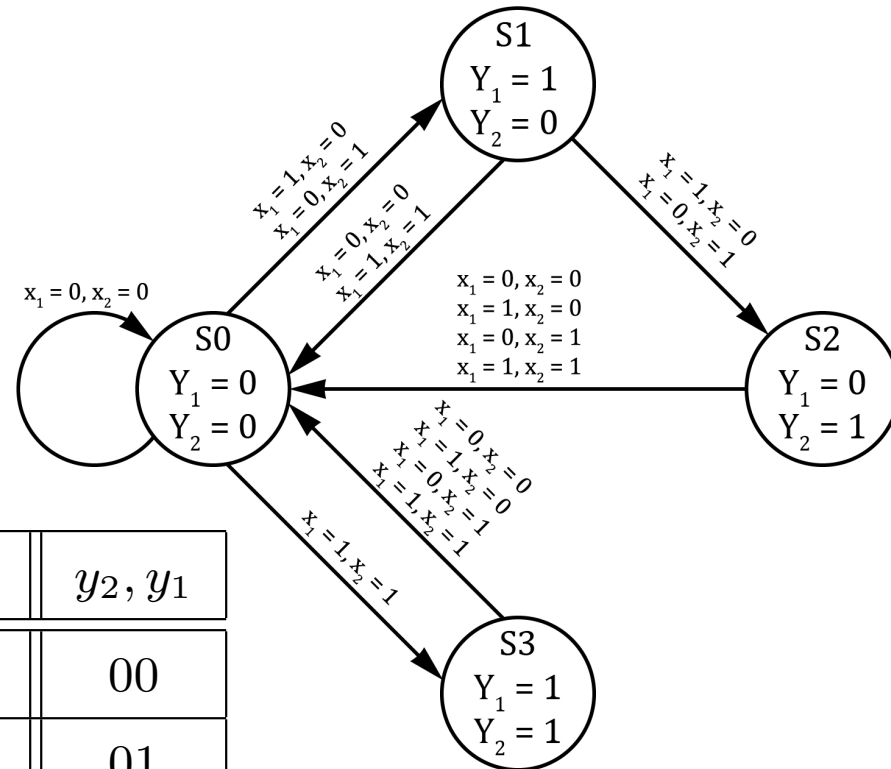

## State coding table

$S^{t+1}$  :

$S^t \backslash x_2, x_1$	00	01	11	10	$y_2, y_1$
$S_0$	$S_0$	$S_1$	$S_3$	$S_1$	00
$S_1$	$S_0$	$S_2$	$S_0$	$S_2$	01
$S_2$	$S_0$	$S_0$	$S_0$	$S_0$	10
$S_3$	$S_0$	$S_0$	$S_0$	$S_0$	11

$Q_1^{t+1}, Q_0^{t+1}$  :

$\frac{x_2, x_1}{Q_1^t, Q_0^t}$	00	01	11	10	$y_2, y_1$
$S_0 \mapsto 00$	00	01	10	01	00
$S_1 \mapsto 01$	00	11	00	11	01
$S_2 \mapsto 11$	00	00	00	00	10
$S_3 \mapsto 10$	00	00	00	00	11

## *Excitation function for D-type flip-flops*

$Q_1^{t+1}, Q_0^{t+1} :$

$\frac{x_2, x_1}{Q_1^t, Q_0^t}$	00	01	11	10	$y_2, y_1$
$S_0 \mapsto 00$	00	01	10	01	00
$S_1 \mapsto 01$	00	11	00	11	01
$S_2 \mapsto 11$	00	00	00	00	10
$S_3 \mapsto 10$	00	00	00	00	11

$D_1 :$

$\frac{x_2, x_1}{Q_1^t, Q_0^t}$	00	01	11	10
00	0	0	1	0
01	0	1	0	1
11	0	0	0	0
10	0	0	0	0

$$D_1 = \overline{Q_1}Q_0\overline{x_2}x_1 + \overline{Q_1}Q_0x_2x_1 + \overline{Q_1}Q_0x_2\overline{x_1}$$

$D_0 :$

$\frac{x_2, x_1}{Q_1^t, Q_0^t}$	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	0	0	0
10	0	0	0	0

$$D_0 = \overline{Q_1}\overline{x_2}x_1 + \overline{Q_1}x_2\overline{x_1}$$

## Output functions

$y_2, y_1 :$

$\frac{x_2, x_1}{Q_1^t, Q_0^t}$	00	01	11	10	$y_2, y_1$
$S_0 \mapsto 00$	00	01	10	01	00
$S_1 \mapsto 01$	00	11	00	11	01
$S_2 \mapsto 11$	00	00	00	00	10
$S_3 \mapsto 10$	00	00	00	00	11

$y_2 :$

$Q_1 \backslash Q_0$	0	1
0	0	0
1	1	1

$$y_2 = Q_1$$


$y_1 :$

$Q_1 \backslash Q_0$	0	1
0	0	1
1	1	0

$$y_1 = \overline{Q_1}Q_0 + Q_1\overline{Q_0} = Q_1 \otimes Q_0$$



## Realization of sequential circuit

 

- Excitation function:  $D_0 = \overline{Q_1}\overline{x_2}x_1 + \overline{Q_1}x_2\overline{x_1}$   
 $D_1 = \overline{Q_1}Q_0\overline{x_2}x_1 + \overline{Q_1}Q_0x_2x_1 + \overline{Q_1}Q_0x_2\overline{x_1}$
- Output function:  $y_2 = Q_1$   
 $y_1 = \overline{Q_1}Q_0 + Q_1\overline{Q_0} = Q_1 \otimes Q_0$

## State coding

The proper choice of coding is important to obtain simple *excitation function*. Unfortunately there is no general method to minimize *excitation function*. We can try to do that follow the rules (according to priority):

- **Rule 1:** - Codes of states, which have the same successor (next state), should differ only one bit,
- **Rule 2:** - Codes of states, which have the same predecessor (previously state), should differ only one bit,
- **Rule 3:** - Codes of states, which have the same outputs under the influence of the same inputs, should differ only one bit.

## State minimization - equivalence of states

Two states are *equivalent* (and can be replaced with one state) if the following conditions are satisfied:

1. Outputs, associated with two states, are the same,
2. All successors of these two states are the same or *equivalent*.

## State minimization - example

$S^t \backslash x_2, x_1$	00	01	11	10	Y - wyjście
1	5	3	2	1	0
2	5	3	1	4	0
3	3	4	4	5	1
4	5	3	2	2	0
5	6	7	1	1	0
6	3	3	1	7	0
7	7	1	1	5	1

- There are not identical states,
- Candidates for *equivalent states*:  $\{1, 2\}$ ,  $\{1, 4\}$ ,  $\{1, 5\}$ ,  $\{1, 6\}$ ,  $\{2, 4\}$ ,  $\{2, 5\}$ ,  $\{2, 6\}$ ,  $\{3, 7\}$ ,  $\{4, 5\}$ ,  $\{4, 6\}$ ,  $\{5, 6\}$ ,
- *Equivalent states*: 3 with 7 and states: 1, 2, 4, 5 and 6.

## State minimization - choice of equivalent states

$S^t \backslash x_2, x_1$	00	01	11	10	Y - output
1	5	3	2	1	0
2	5	3	1	4	0
3	3	4	4	5	1
4	5	3	2	2	0
5	6	7	1	1	0
6	3	3	1	7	0
7	7	1	1	5	1

candidates	second condition of equ.	Non-equivalence	1 iteration	2 iteration
{1, 2}	{1, 2}, {1, 4}			
{1, 4}	{1, 2}			
{1, 5}	{5, 6}, {3, 7}, {1, 2}	Non-equivalent		see {5, 6}
{1, 6}	{3, 5}, {1, 2}, {1, 7}	Non-equivalent	see {3, 5}	
{2, 4}	{1, 2}, {2, 4}			
{2, 5}	{5, 6}, {3, 7}, {1, 4}	Non-equivalent		see {5, 6}
{2, 6}	{3, 5}, {4, 7}	Non-equivalent	see {3, 5}	
{3, 7}	{3, 7}, {1, 4}			
{4, 5}	{5, 6}, {3, 7}, {1, 2}	Non-equivalent		see {5, 6}
{4, 6}	{3, 5}, {1, 2}, {2, 7}	Non-equivalent	see {3, 5}, {2, 7}	
{5, 6}	{3, 6}, {3, 7}, {1, 7}	Non-equivalent	see {3, 6}, {1, 7}	

- A - states {1, 2, 4} B - states {3, 7} C - state {5} D - state {6}

## State minimization - reduced table

- A - stats {1, 2, 4} B - stats {3, 7} C - state {5} D - state {6}

$S^t \backslash x_2, x_1$	00	01	11	10	Y - output
1	5	3	2	1	0
2	5	3	1	4	0
3	3	4	4	5	1
4	5	3	2	2	0
5	6	7	1	1	0
6	3	3	1	7	0
7	7	1	1	5	1

$S^t \backslash x_2, x_1$	00	01	11	10	Y - output
<i>A</i>	<i>C</i>	<i>B</i>	<i>A</i>	<i>A</i>	0
<i>B</i>	<i>B</i>	<i>A</i>	<i>A</i>	<i>C</i>	1
<i>C</i>	<i>D</i>	<i>B</i>	<i>A</i>	<i>A</i>	0
<i>D</i>	<i>B</i>	<i>B</i>	<i>A</i>	<i>B</i>	0

## Systems fully not determined

In the case of system which are not fully determined

- The one or more of input combination is not determined - e.g. slide 11, point 3 when system would count *mod*3 only due to input combination  $x_2x_1 = 10$  (for input combination  $x_2x_1 = 01$  system would not be determined),
- During coding states we obtain redundant states - e.g. counter *mod*3 (needs 3 states, which can be realized with 2 flip-flops - total states 4, 1 redundant)

If state is not determined we can put instead that state any value we want.

## Mealy's state machine - remarks

- In *Mealy's machine state* state is not unequivocally related to output,
- For that reason it is possible reduce the potential number of states at the cost of more complicated output function,
- System diagram should take into consideration input-output dependencies.



## Task for laboratory

1. Design and realize traffic lights for vehicles. System should work in two modes:
  - *normal mode* - Input is equal 1. On output there is a sequence of lights  
 $red \rightarrow red + yellow \rightarrow green \rightarrow yellow$
  - *emergency mode* - 0 given on input causes **continuous yellow light on output**.
2. Design and realize traffic lights for vehicles. System should work in two modes:
  - *normal mode* - Input is equal 1. On output blinks as follow:  
 $red \rightarrow red + yellow \rightarrow green \rightarrow yellow$
  - *emergency mode* - 0 given on input causes **blinking yellow light on output**.

Clock in emergency mode should be 8 times bigger then in normal.