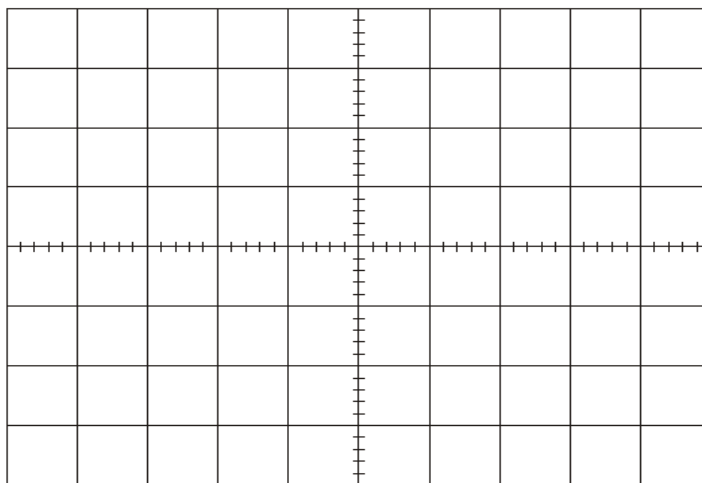


Lab. 2	Passive elements measurement				Date:
name and surname			points	Supervisor	

1. Resistor impedance - observation and measurement of time dependence between current and voltage on resistor.

Draw current and voltage on the resistor (measuring module M2, R1R, frequency $f = 100\text{kHz}$, WE-voltage, WY-current).



Calculate:

A. Phase shift (phase ϕ) between voltage and current :

Period T : [number of divisions]	Shift t_p [Number of divisions]	Phase [$\phi = \frac{t_p}{T} 360^\circ$]

B. Calculate the impedance module $|Z|$

U_{pp} number of divisions	Sensitivity	U_{pp}	I_{pp} number of divisions	Sensitivity	U_{Ipp}	$I_{pp} = \frac{U_{Ipp}}{10\Omega}$	$ Z = \frac{U_{pp}}{I_{pp}}$
[div]	[V/div]	[V]	[div]	[V/div]	[V]	[A]	[Ω]

I_{pp} - the current is measured by measuring the voltage drop U_{Ipp} on the resistor 10Ω

C. Calculate impedance:

$$Z = |Z| e^{j\phi} = \dots = R + jX = \dots + j \dots$$

Polish Japanese Academy of Information Technology


2. Determination of capacitor impedance

Draw the currents and voltages on the capacitor.

(measurement module M2 CR switch, frequency $f = 100\text{kHz}$, WE-voltage, WY-current).

Calculate:

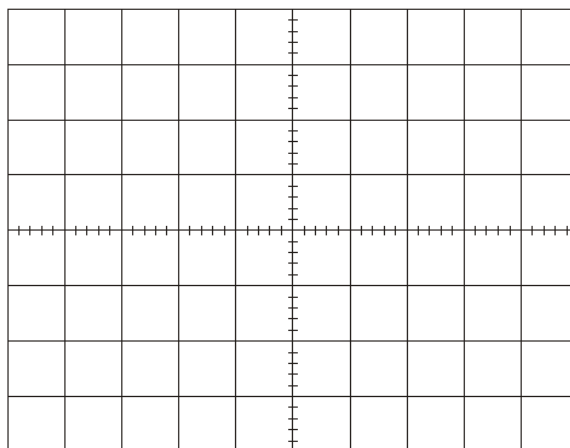A. Phase shift ϕ between voltage and current




Period T : [number of divisions]	Shift tp [Number of divisions]	Phase [$\phi = \frac{tp}{T} 360^\circ$]

B. Calculate the impedance module $|Z|$

U_{pp} num. of div.	Sensitivity	U_{pp}	I_{pp} num. of div.	Sensitivity	U_{Ipp}	$I_{pp} = \frac{U_{Ipp}}{10 \Omega}$	$ Z = \frac{U_{pp}}{I_{pp}}$
[div]	[V/div]	[V]	[div]	[V/div]	[V]	[A]	[Ω]

C. Calculate the impedance of the capacitor:

$$Z = |Z| e^{j\phi} = \dots\dots\dots = R - jX = \dots\dots\dots - j \dots\dots\dots$$

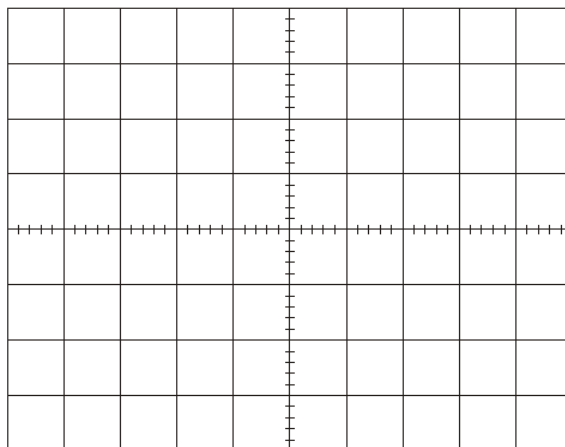

3. Determination of inductor impedance

Draw the currents and voltages on the capacitor.

(measurement module M2 LR switch, frequency $f = 100\text{kHz}$, WE-voltage, WY-current).

Calculate:

A. Phase shift ϕ between voltage and current

Period T : [number of divisions]	Shift tp [Number of divisions]	Phase [$\phi = \frac{tp}{T} 360^\circ$]

B. Calculate the impedance module $|Z|$

U_{pp} num. of div.	Sensitivity	U_{pp}	I_{pp} num. of div.	Sensitivity	U_{Ipp}	$I_{pp} = \frac{U_{Ipp}}{10 \Omega}$	$ Z = \frac{U_{pp}}{I_{pp}}$
[div]	[V/div]	[V]	[div]	[V/div]	[V]	[A]	[Ω]

C. Calculate inductor impedance:

$$Z = |Z| e^{j\phi} = \dots\dots\dots = R + jX = \dots\dots\dots + j \dots\dots\dots$$