

Lab. 5	<b>Operational amplifiers</b>		Date:
name and surname		points	Supervisor

### 1. Offset voltage measurement.

$$U_{\text{Offsetvoltage}} = \dots\dots\dots [mV]$$

### 2. Open loop output voltage measurement

$$U_{\text{Open}} = \dots\dots\dots [V]$$

Explain points 1 and 2:

### 3. Parameters of inverting operational amplifiers measurement

Find gain and input resistance of inverting amplifier

$U_{\text{in}}$	$U_{\text{in}^-}$	$U_{\text{out}}$	$R_1$	$k_U$	$R_{\text{in}}$
[V]	[mV]	[V]	[kΩ]	[V/V]	[kΩ]
notes				$k_U = \frac{U_{\text{out}}}{U_{\text{in}}}$	$R_{\text{in}} = \frac{U_{\text{in}}}{I_{\text{in}}}$

$$I_{\text{in}} = \frac{U_{\text{in}} - U_{\text{in}^-}}{R_1}$$

### 4. Parameters of noninverting operational amplifiers measurement

Find gain and input resistance of noninverting amplifier

$U_{\text{in}}$	$U_{\text{in}^+}$	$U_{\text{out}}$	$R_3$	$k_U$	$R_{\text{in}}$
[V]	[V]	[V]	[kΩ]	[V/V]	[MΩ]
notes				$k_U = \frac{U_{\text{out}}}{U_{\text{in}}}$	$R_{\text{in}} = \frac{U_{\text{in}}}{I_{\text{in}}}$


$$I_{\text{in}} = \frac{U_{\text{in}} - U_{\text{in}^+}}{R_3}$$

5. Slew rate measurement

	a	sensitivity	$\Delta U$	b	Time base	$\Delta t$	Slew rate
	[div]	[V/div]	[V]	[div]	$[\frac{\mu s}{div}]$	$[\mu s]$	$[\frac{V}{\mu s}]$
rising							
falling							
notes							$SR = \frac{\Delta U}{\Delta t}$

6. Inverting operational amplifier magnitude characteristic

f	a	Sa	$U_{in}$	b	Sb	$U_{out}$	k	$k_{dB}$
[Hz]	[div]	[V/div]	[V]	[div]	[V/div]	[V]	[V/V]	[dB]

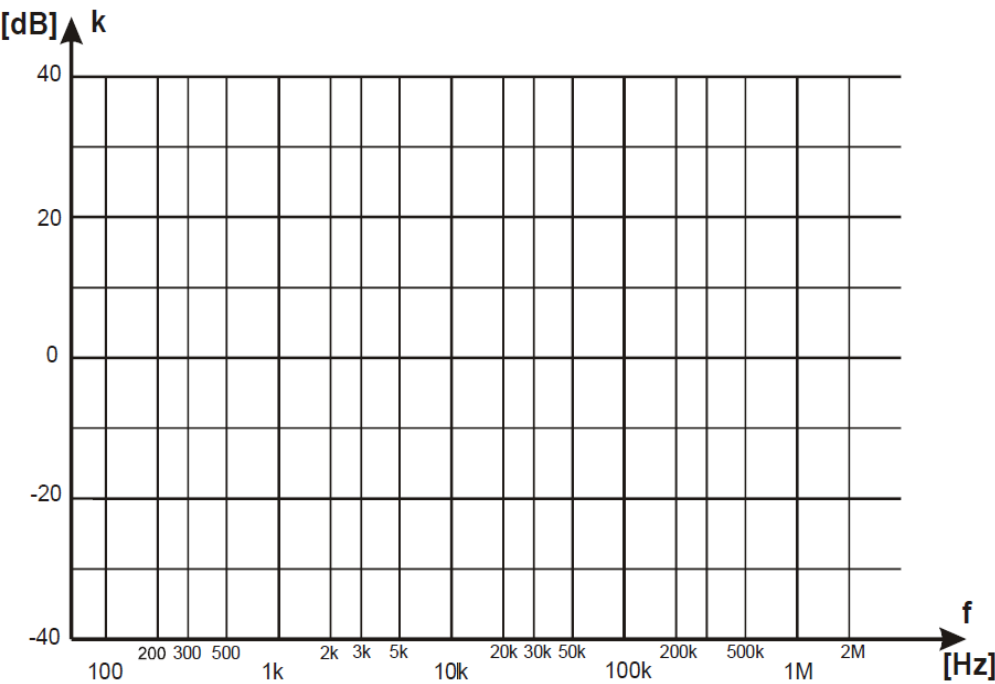

$f_{cut} = \dots\dots\dots$