

# Digital systems and basics of electronics


Adam Szmigielski

aszmigie@pjwstk.edu.pl

materials: *ftp(public) : //aszmigie/SYC/ENG*

# Sequential Circuits - introduction - lecture 9


## Combinational circuits

 

układ kombinacyjny


- *Combinational circuits* outputs depend only on inputs.

## Flip-flops and “memory effect”

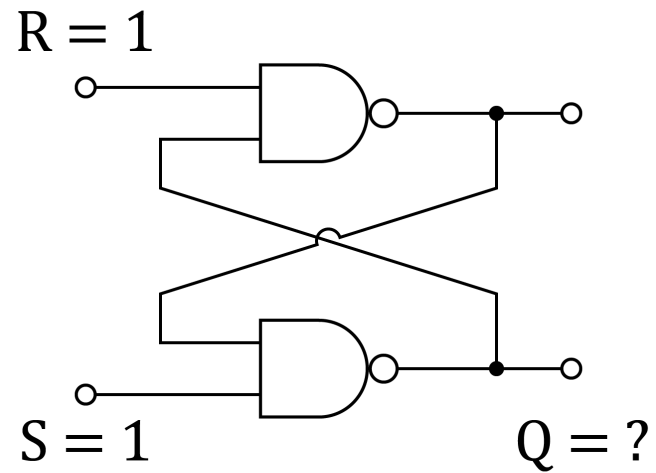

What is the current value of output  $Q$  ?


## Feedback and “memory effect”

 


- In closed feedback loop system *output* influences *input*,
- That influence is an reason, why output depends not only on inputs, but also on history of outputs.

# Combinational and sequential circuits

układ kombinacyjny

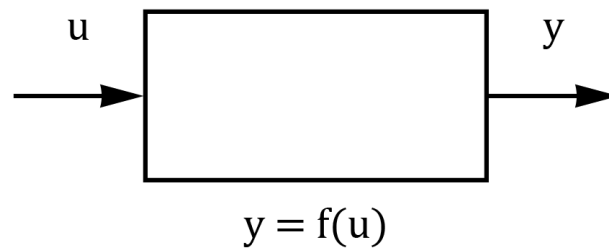

układ sekwencyjny

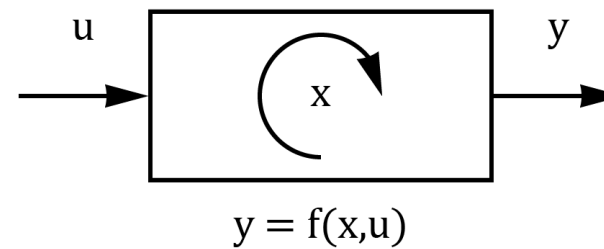


## Sequential circuit as dynamical system

$$\begin{cases} x(k+1) = a \cdot x(k) + b \cdot u(k) & \text{state equation} \\ y(k) = c \cdot x(k) + d \cdot u(k) & \text{output equation} \end{cases}$$


- *sequential* (dynamical) system there is *internal state*,
- *Internal state* can not be changed as one wishes". The value of current state depends on previously,
- *Internal state* can be not visible on system output (because is "internal").

## Mealy's and Moore's automata

automat Mealy's

 

automat Moore's

 


Output function is realized by combinational block ( $\lambda$ ) and block ( $\delta$ ) realizes memory (sequential circuit).



## RS flip-flop

$S_t$	$R_t$	$Q_{t+1}$
0	0	<i>forbidden</i>
0	1	1
1	0	0
1	1	$Q_t$ ( <i>previously</i> )

 

$$Q_{t+1} = Q_t \cdot R_t + \overline{S}_t$$

- *Flip-flops* are the main components to build *sequential circuits*.


## Clock - the way to synchronize changes



- The sequence of states is important in sequential circuits,
- Additional signal called *clock* is used to synchronize changes,
- Clock input can be activated by *state* (level) or *slope* (level change).

## Clock activated with level


$S$	$R$	$Q_{t+1}$
0	0	$Q_t$
0	1	0
1	0	1
1	1	<i>forbidden</i>

 

- If clock signal is equal zero  $C = 0$  signals  $R$  and  $S$  have no any influence on output  $Q$ .
- If clock signal is equal one  $C = 1$  output  $Q$  changes due to the table,
- the change of clock signal  $C$  from 1 to 0 causes the latch of output state - for that reason that circuit is sometimes called *latch*.

## Type D flip-flop

$D_t$	$Q_{t+1}$
0	0
1	1

 


$$Q_{t+1} = D_t$$

- Output  $Q$  changes follow input  $D$ ,
- Flip-flop has two states.
- Changes are synchronized with clock slope  $C$ ,
- Flip-flop has asynchronous clearing input (CLR) and setting input (SET). Both inputs work independently on clock (immediately clears or sets output  $Q$ ).

## Type J-K flip-flop

$J_t$	$K_t$	$Q_{t+1}$
0	0	$Q_t$
0	1	0
1	0	1
1	1	$\overline{Q_t}$

 


$$Q_{t+1} = J_t \cdot \overline{Q_t} + \overline{K_t} \cdot Q_t$$

- Flip-flop has two states.
- Changes are synchronized with clock slope  $C$ ,
- Flip-flop has asynchronous inputs - clearing (CLR) and setting (SET).

## Type T flip-flop


$T_t$	$Q_t$	$Q_{t+1}$
0	0	0
0	1	1
1	0	1
1	1	0

 

$$Q_{t+1} = T_t \oplus Q_t$$


- In T-type flip-flop logical one on input causes that flip flop will change the state of output,
- Logical 0 on input T cause keeping the state of output.

# Register

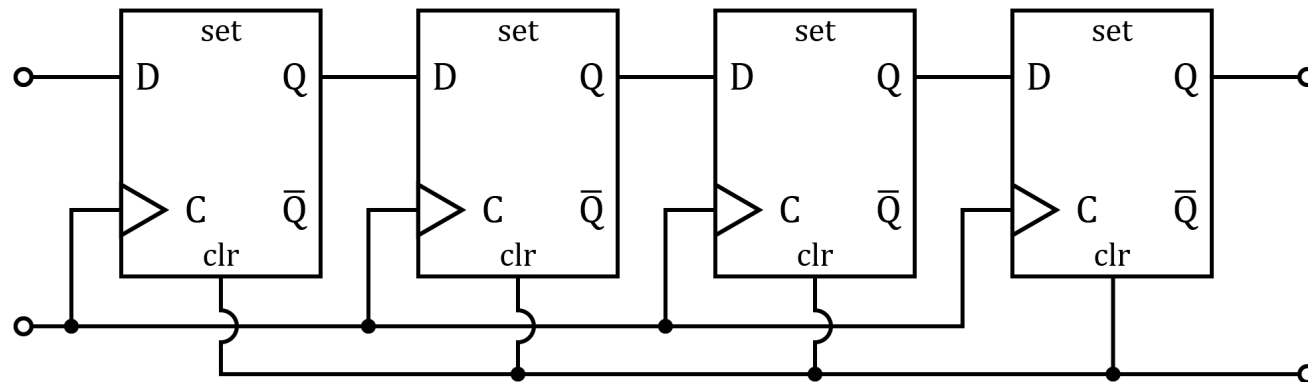

4-bits shifting register.


## Ring counter

 

A ring counter is a type of counter composed of a circular shift register.




## Twisted ring - Johnson counter

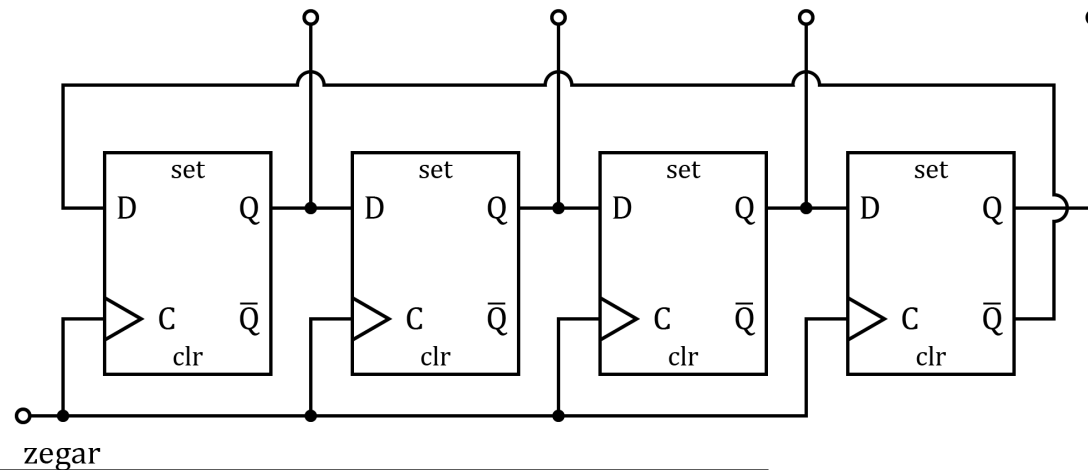


Wartość dziesiętna	Wartość binarna	Kod Johnsona
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0111
4	0100	1111
5	0101	1110
6	0110	1100
7	0111	1000
 
## Pseudo-random signal generator using shift register



Generated signal seems to be randomly.



## PRBS generator using shift register

 

*Pseudo Random Binary Signal* generator using 8-bits shift register.


- **PRBS must be initialized with ones**
- For  $T/T_o = 255$  bits: 2, 3, 4, 8,
- for  $T/T_o = 1023$  bts: 7, 10.
 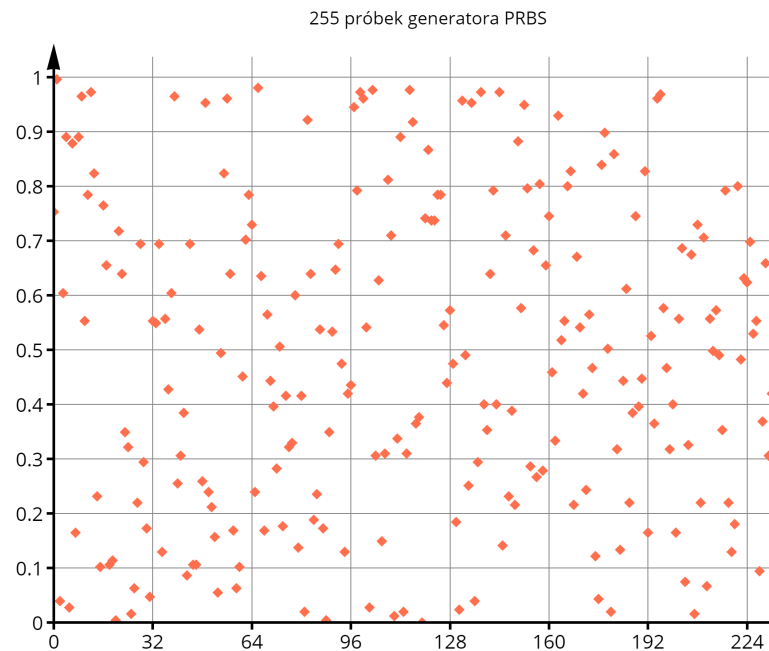
## Results of PRBS for 255 and 1255 samples




- PRBS is periodical

## Frequency divider 2

 


- J-K flip-flop can be used as frequency divider when both input are logically "1",
- Similar way works D-type flip-flop when to the input *D* is connected signal from negated output  $\overline{Q}$ .

## Forward counter

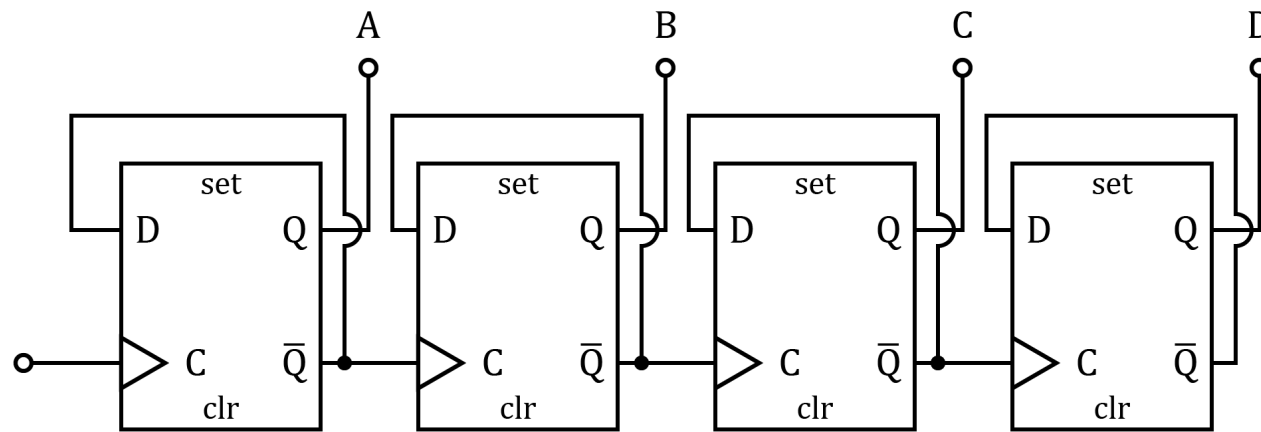


4-bits forward counter.

## Modulo counter

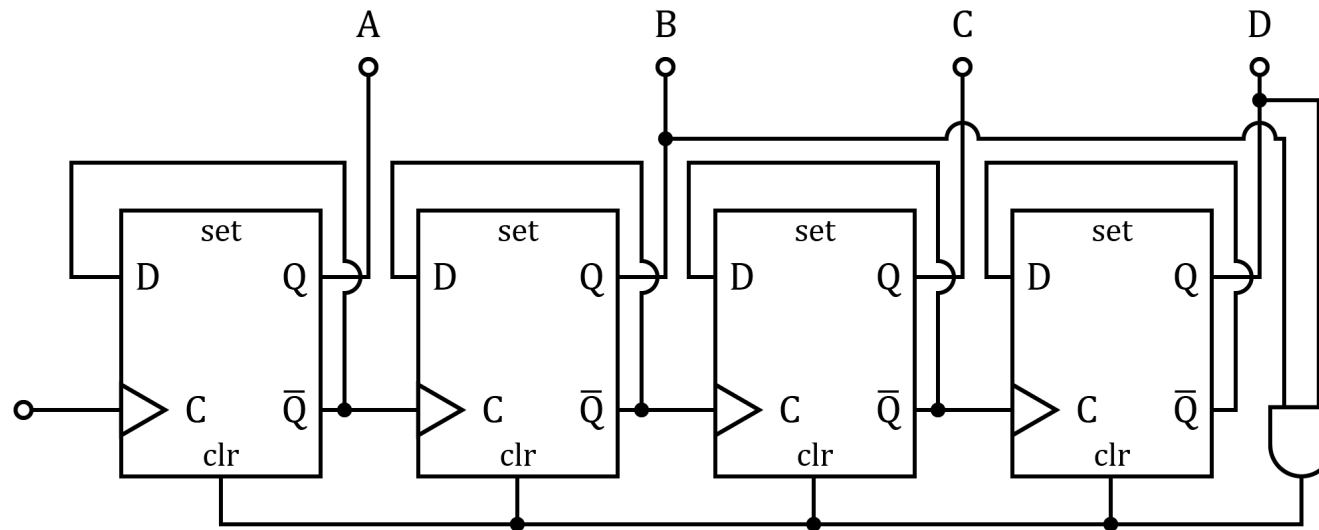

Asynchronous counter *mod*10

## Counter - setting input

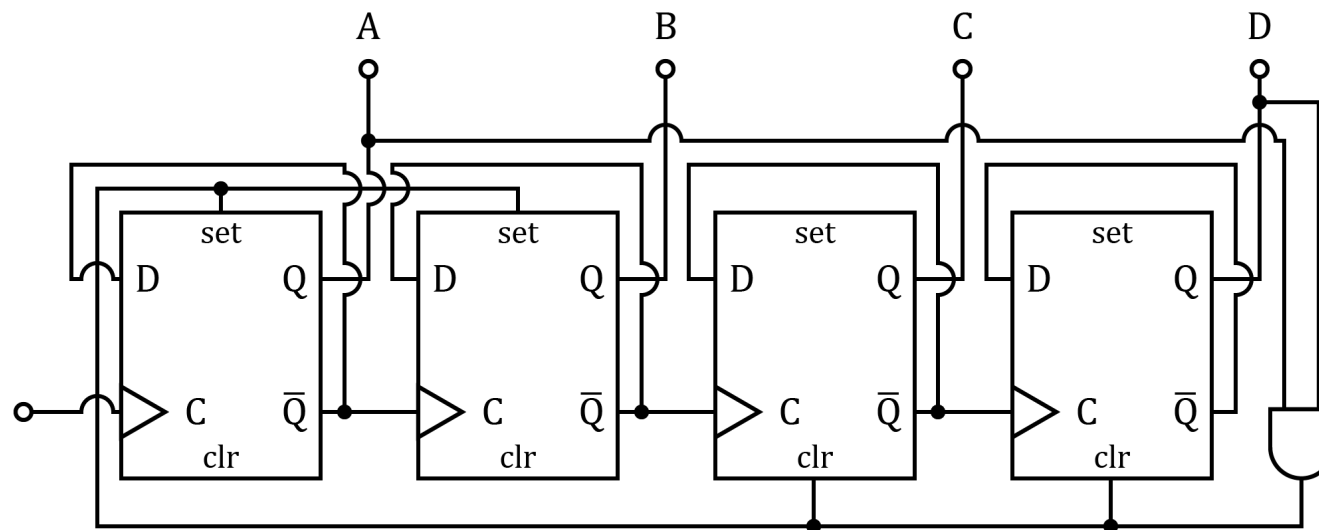

Asynchronic counter realizes sequence  $3 - 4 - 5 - 6 - 7 - 8$ .



## Tasks for laboratory

1. Using D-type flip-flops build 4-bit *shift register*,
2. Using *shift register* from point 1. build ring counter,
3. Using *shift register* from point 1. build Johnson counter,
4. Using D-type flip-flops build *mod9 counter*,
5. Using D-type flip-flops build counter from 3 to 9,
6. Using *shift register* from point 1. and XOR logic gate make PRBS *Pseudo Random Binary Signal* generator.
7. Build, in a separate circuit, the 1-bit latch using the RS flip-flops built from the NAND gates.
8. Implement the 4-bit serial shift register, in the possibility of parallel writing out and latching the state of the registry. The latch can be used from the previous point